



Electrical and Computer Engineering Department

ENCS3310

ADVANCED DIGITAL SYSTEMS DESIGN

Project Report

Design a 2-digit BCD adder (8 bits)

Instructor: Dr. Abdallatif Abulssa.

Section: 1.

Student's Name: Saif Battah.

Student's ID: 1170986.

Introduction & Abstract

In this project we're going to create a 2-digit "BCD" adder.

We will use Verilog coding language using "Aldec" program to implement the code.

We will create this system using 1-bit full adder, 4-bit binary adder, 1-bit "BCD" adder and Registers.

So our program should work as "ADDING" Calculator, for example: if we tend to set **A = 54**, **B = 34**, so our program should add these numbers starting from Least significant bit which are **AL = 4**, **BL = 4** and give us a Least Sum which is **SL = 8**; and set carry to **0** or **1** depending whether the **SL** is less than or greater than **9** "IF **SL > 9** → set carry to **1**, else carry = **0**", then after we finish the least significant we move to add the most significant with the carry from the least operation, which are **AM = 5**, **BM = 3**, **Carry = 0**, so the Most significant sum is **8**.

After that we combine "not adding" the least sum with the most sum and final carry to get the adding result which is **88**.

And as I mentioned before I've built the system using these smaller system:

- Built 1-bit full adder from the basic gates.
- Use the full adder to build 4-bit adder.
- Use the 4-bit adders to build 1-Digit BCD Adder.
- Use the 1-Digit BCD Adder to build the 2-Digit BCD Adder

Also we have these delays to be used when we use a specific gate


Gate	Delay
Inverter	3 ns
NAND	6 ns
NOR	6 ns
AND	8 ns
OR	8 ns
XNOR	10 ns
XOR	12 ns

Finally, after building the whole system we have to go over 2 stages, each stage has its own specification to test the output results and searching for any error in the adding process, so we will test 2^{16} situations to check the validity and accuracy of our system.


Program Design

Starting with basic gates:


1. And Gate

 


2. Or Gate

 

3. XOR Gate

 


Full Adder (1-bit)

 

Code

```
module FA_1bit(A,B,Cin,Sum,Cout);  
  
    input A,B,Cin;  
    output Sum,Cout;  
    wire w1,w2,w3;  
  
    and #(8ns) (w1,A,B);  
    xor #(12ns) (w2,A,B);  
    and #(8ns) (w3,w2,Cin);  
    xor #(12ns) (Sum,w2,Cin);  
    or #(8ns) (Cout,w1,w3);  
  
endmodule
```


Binary Adder (4-bit)

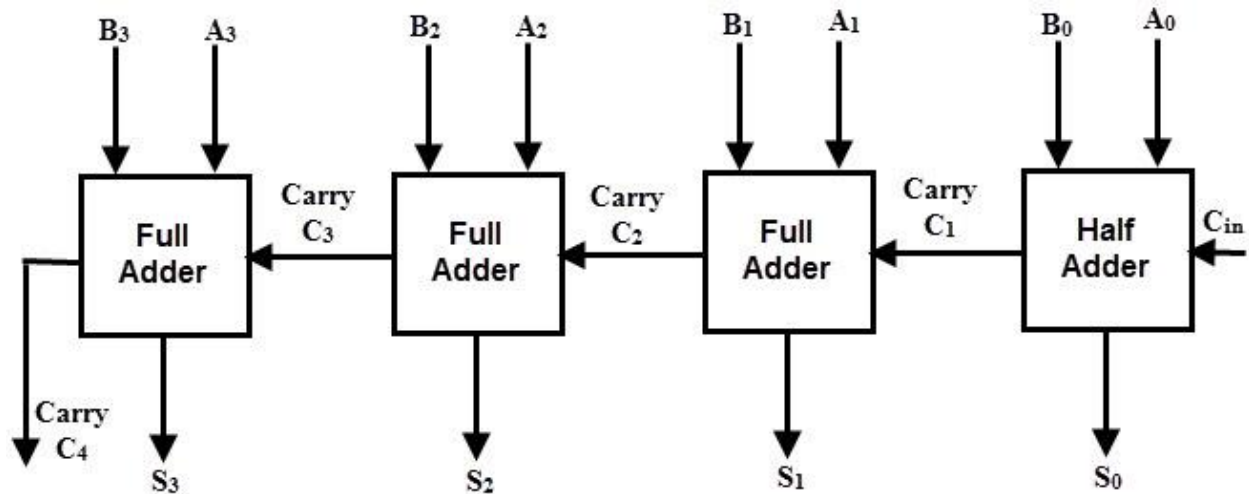

Code

```
module BinaryAdder_4bit(A,B,Cin,Sum,Cout);  
  
    input [3:0] A,B;  
    input Cin;  
    output [3:0] Sum;  
    output Cout;  
    wire C1,C2,C3;  
  
    FA_1bit F1(A[0],B[0],Cin,Sum[0],C1);  
    FA_1bit F2(A[1],B[1],C1,Sum[1],C2);  
    FA_1bit F3(A[2],B[2],C2,Sum[2],C3);  
    FA_1bit F4(A[3],B[3],C3,Sum[3],Cout);  
  
endmodule
```

BCD Adder (1-bit)

 

Code

```

module BCD_Adder1bit(A,B,Cin,F,OutputCarry);
    input [3:0] A,B;
    input Cin;
    output [3:0] F;
    output OutputCarry;
    wire [3:0] Z,S;
    wire k,w1,w2,w3;


    BinaryAdder_4bit BA1(A,B,Cin,Z,k);

    and #(8ns) (w1,Z[2],Z[3]);
    and #(8ns) (w2,Z[1],Z[3]);
    or  #(8ns) (OutputCarry,k,w1,w2);

    assign S = {1'b0,OutputCarry,OutputCarry,1'b0};
    BinaryAdder_4bit BA2(Z,S,0,F,w3);
endmodule

```


D Flip Flop

 

Code

```
module dff(Q,D,clk);  
    input D,clk;  
    output reg Q;  
  
    always @(posedge clk)  
        begin  
            Q <= D;  
        end  
endmodule
```


Input Register

 

Code

```
module Register_input(out,in,clk);
    output reg [7:0] out;
    input [7:0] in;
    input clk;
    wire [7:0] temp_out;

    dff d0(temp_out[0],in[0],clk);
    dff d1(temp_out[1],in[1],clk);
    dff d2(temp_out[2],in[2],clk);
    dff d3(temp_out[3],in[3],clk);
    dff d4(temp_out[4],in[4],clk);
    dff d5(temp_out[5],in[5],clk);
    dff d6(temp_out[6],in[6],clk);
    dff d7(temp_out[7],in[7],clk);

    always @ (posedge clk)
        begin
            out = temp_out;
        end
endmodule
```

Output Register




Code

```
module Register_output(out,in,clk);
    output reg [8:0] out;
    input [8:0] in;
    input clk;
    wire [8:0] temp_out;

    dff d0(temp_out[0],in[0],clk);
    dff d1(temp_out[1],in[1],clk);
    dff d2(temp_out[2],in[2],clk);
    dff d3(temp_out[3],in[3],clk);
    dff d4(temp_out[4],in[4],clk);
    dff d5(temp_out[5],in[5],clk);
    dff d6(temp_out[6],in[6],clk);
    dff d7(temp_out[7],in[7],clk);
    dff d8(temp_out[8],in[8],clk);

    always @ (posedge clk)
        begin
            out = temp_out;
        end
endmodule
```

The Whole System Structurally

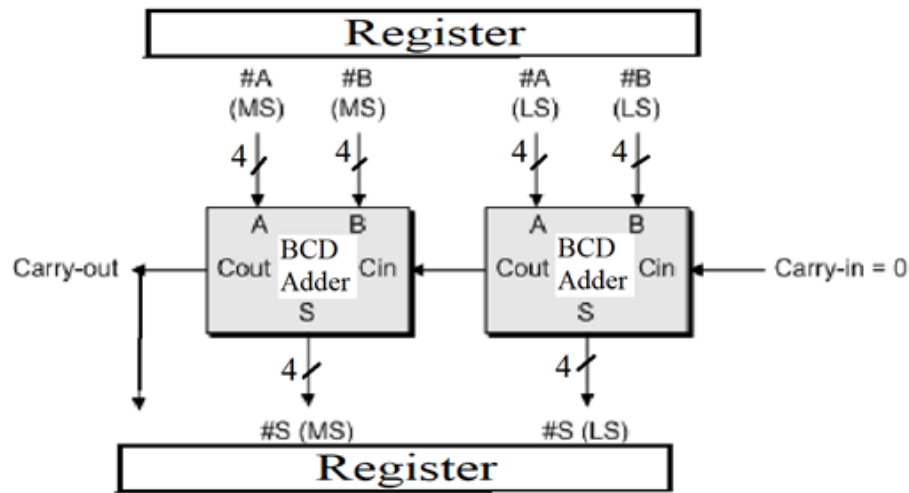

Code

```

module System(A,B,clk,Result);
    input [7:0] A,B;
    reg Carryout;
    output reg [8:0] Result;
    reg [7:0] Aout,Bout;
    reg tempCout,tempCin;
    input clk;
    reg [3:0] SL,SM,AL,BL,AM,BM;
    reg [8:0] tempResult;

    Register_input IA(Aout,A,clk);
    Register_input IB(Bout,B,clk);

    assign AL = Aout[3:0];
    assign BL = Bout[3:0];
    assign AM = Aout[7:4];
    assign BM = Bout[7:4];

    BCD_Adder1bit D1(AL,BL,1'b0,SL,tempCout);

    assign tempCin = tempCout;

    BCD_Adder1bit D2(AM,BM,tempCin,SM,Carryout);

    always @ (posedge clk)
        begin
            assign tempResult = {Carryout,SM,SL} ;
        end

    Register_output O(Result,tempResult,clk);
endmodule

```

BCD Tester for Stage 1

Which is a "BCD" behavioral code


```
module BCD_Tester(A,B,Result);
    input [7:0] A,B;
    output reg [8:0] Result;
    reg [7:0] Sum;
    reg Cout;

    reg [3:0] AL,AM,BL,BM,SL,SM;
    reg temp_carry;
    reg [4:0] temp_SL,temp_SM;

    assign AL = A[3:0];
    assign BL = B[3:0];
    assign AM = A[7:4];
    assign BM = B[7:4];

    always @ (*)
    begin
        temp_SL = AL + BL + 0;
        if(temp_SL > 9)
            begin
                temp_SL = temp_SL + 6;
                temp_carry = 1;
                SL = temp_SL[3:0];
            end
        else
            begin
                temp_carry = 0;
                SL = temp_SL[3:0];
            end
        temp_SM = AM + BM + temp_carry;
        if(temp_SM > 9)
            begin
                temp_SM = temp_SM + 6;
                Cout = 1;
                SM = temp_SM[3:0];
            end
        else
            begin
                Cout = 0;
                SM = temp_SM[3:0];
            end
        Sum = {SM,SL};
        #700ns Result = {Cout,Sum};
    end
endmodule
```

Stage 1

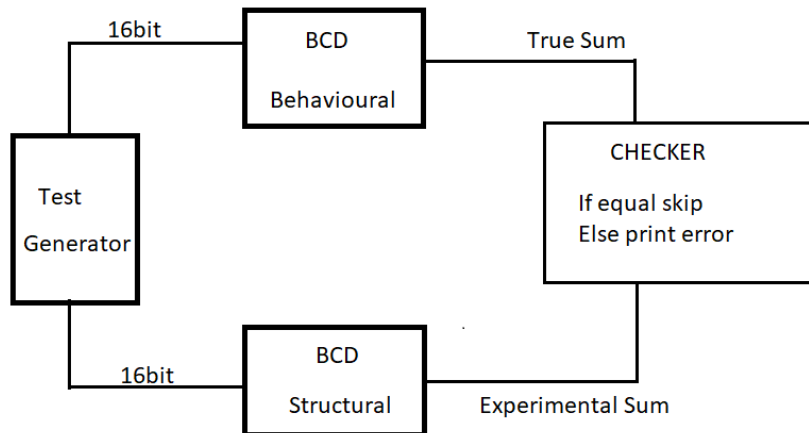

Code

```
module Stage_1();
    reg [7:0] A,B;
    reg clk;
    wire [8:0] True_Result,Exp_Result;


    System S1(A,B,clk,Exp_Result); //Experimental Sum
    BCD_Tester T1(A,B,True_Result); //True Sum

    always #(100ns) clk = ~clk;

    initial
        begin
            clk = 0;
            {B,A} = 16'b0000000000000000;
            #700ns {B,A} = 16'b0000000000000000;

            repeat(65535)
                #(900ns) {B,A} = {B,A} + 16'b0000000000000001;
            if(Exp_Result != True_Result)
                begin
                    $display ("Error! at %b",True_Result);
                end
        end
end
endmodule
```

Carry look ahead adder (4-bit)

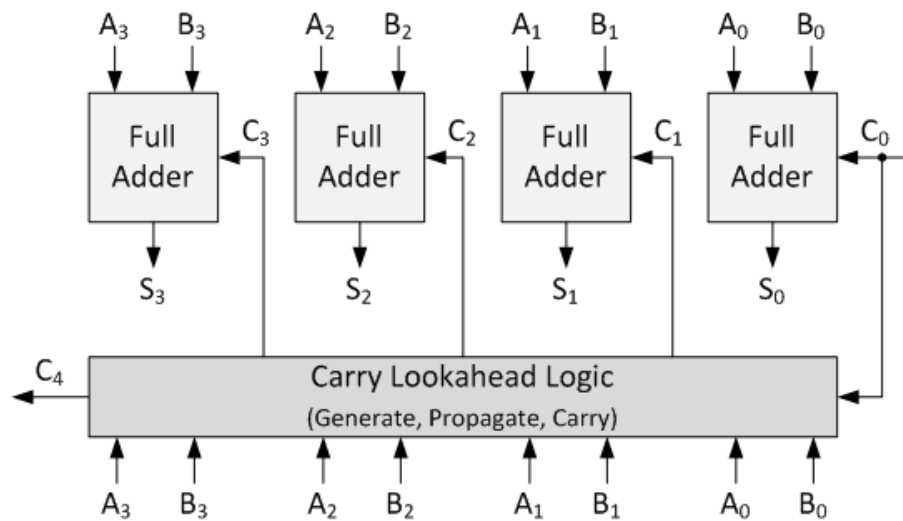

Code

```
module carry_lookahead_adder_4_bit(i_add1, i_add2, o_result);
    input [3:0] i_add1, i_add2;
    output [4:0] o_result;
    wire [4:0] w_C;
    wire [3:0] w_G, w_P, w_SUM;

    FA_lbit F1(.A(i_add1[0]), .B(i_add2[0]), .Cin(w_C[0]), .Sum(w_SUM[0]), .Cout());
    FA_lbit F2(.A(i_add1[1]), .B(i_add2[1]), .Cin(w_C[1]), .Sum(w_SUM[1]), .Cout());
    FA_lbit F3(.A(i_add1[2]), .B(i_add2[2]), .Cin(w_C[2]), .Sum(w_SUM[2]), .Cout());
    FA_lbit F4(.A(i_add1[3]), .B(i_add2[3]), .Cin(w_C[3]), .Sum(w_SUM[3]), .Cout());

    assign w_G[0] = i_add1[0] & i_add2[0];
    assign w_G[1] = i_add1[1] & i_add2[1];
    assign w_G[2] = i_add1[2] & i_add2[2];
    assign w_G[3] = i_add1[3] & i_add2[3];

    assign w_P[0] = i_add1[0] | i_add2[0];
    assign w_P[1] = i_add1[1] | i_add2[1];
    assign w_P[2] = i_add1[2] | i_add2[2];
    assign w_P[3] = i_add1[3] | i_add2[3];

    assign w_C[0] = 1'b0;
    assign w_C[1] = w_G[0] | (w_P[0] & w_C[0]);
    assign w_C[2] = w_G[1] | (w_P[1] & w_C[1]);
    assign w_C[3] = w_G[2] | (w_P[2] & w_C[2]);
    assign w_C[4] = w_G[3] | (w_P[3] & w_C[3]);

    assign o_result = {w_C[4], w_SUM};
endmodule
```

Look Ahead BCD Adder (1-bit)

Code

```
module BCD_Adder_LA_1bit(A,B,F);
    input [3:0] A,B;
    output [4:0] F;
    reg [3:0] tempF;
    reg [3:0] Z,S;
    reg tempc;

    carry_lookahead_adder_4_bit BA1(A,B,S);

    always @(*)
    if( S > 4'b1001)
        begin
            assign Z = 4'b0110;
            assign tempc = 1'b1;
        end
    else
        begin
            assign Z = 4'b0000;
            assign tempc = 1'b0;
        end

    carry_lookahead_adder_4_bit BA2(S,Z,tempF);
    assign F={tempc,tempF};
endmodule
```

Look Ahead BCD Adder (2-bit)

Code

```
module BCD_Adder_LA_2bit(A,B,Result);

    input [7:0] A,B;
    output [8:0] Result;
    reg [4:0] SL,SM;
    reg tens,hunds;

    BCD_Adder_LA_1bit B1(A[3:0],B[3:0],SL);

    assign tens = SL[4];


    BCD_Adder_LA_1bit B2({A[7:4]+tens},B[7:4],SM);

    assign hunds = SM[4];

    assign Result = {hunds,SM[3:0],SL[3:0]};

endmodule
```

Stage2

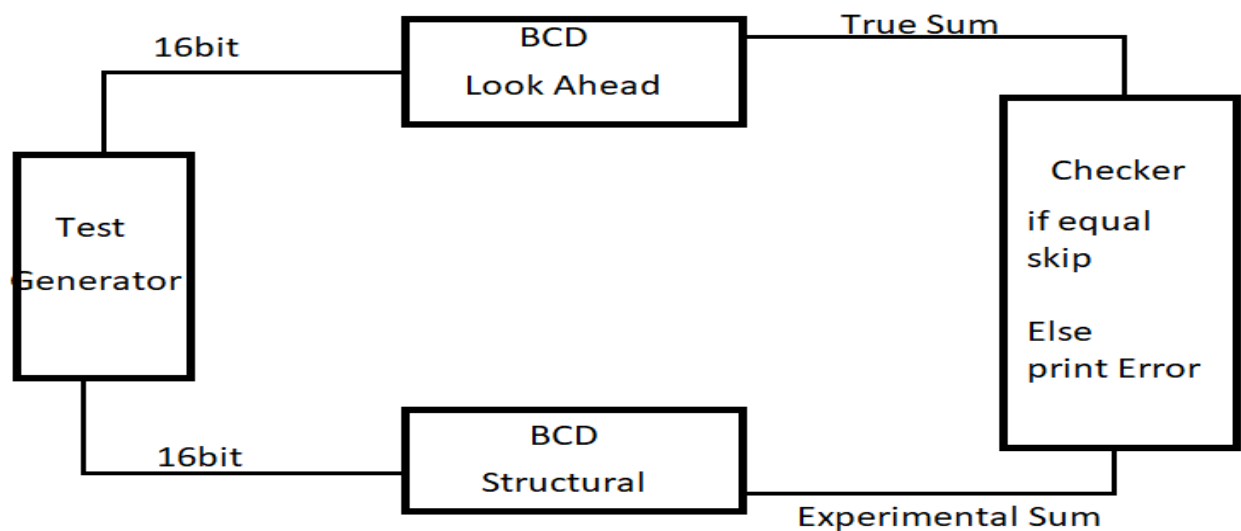

Code

```

module Stage_2();
    reg [7:0] A,B;
    reg clk;
    wire [8:0] True_Result,Exp_Result;

    System S1(A,B,clk,Exp_Result); //Experimental Sum
    BCD_Adder_LA_2bit T1(A,B,True_Result); //True Sum

    always #(100ns) clk = ~clk;

    initial
        begin
            clk = 0;
            {B,A} = 16'b0000000000000000;
            #700ns {B,A} = 16'b0000000000000000;

            repeat(65535)
                #(900ns) {B,A} = {B,A} + 16'b0000000000000001;
            if(Exp_Result != True_Result)
                begin
                    $monitor ("Error! at %b",True_Result);
                end
        end
    end
endmodule
  
```


Results

Stage 1

For this stage I've tried a lot of delay values until I reached the one which gives us the results we need

These delay values are


700ns in ~BCD_Tester~ Result


100ns in clk

700ns for {B,A} = 16'b0000000000000000;

900ns for {B,A} = {B,A} + 16'b0000000000000001;

Screenshots

 

 

Error

After changing delays from 700 ns, an error occur in checker

```
> run 9000000 ns
> # KERNEL: Error! at 101011011
> # KERNEL: stopped at time: 9 ms
> 101101
```

Stage 2

For this stage I've tried a lot of delay values until I reached the one which gives us the results we need


These delay values are

100ns in clk

700ns for {B,A} = 16'b0000000000000000;

900ns for {B,A} = {B,A} + 16'b0000000000000001;

Screenshots

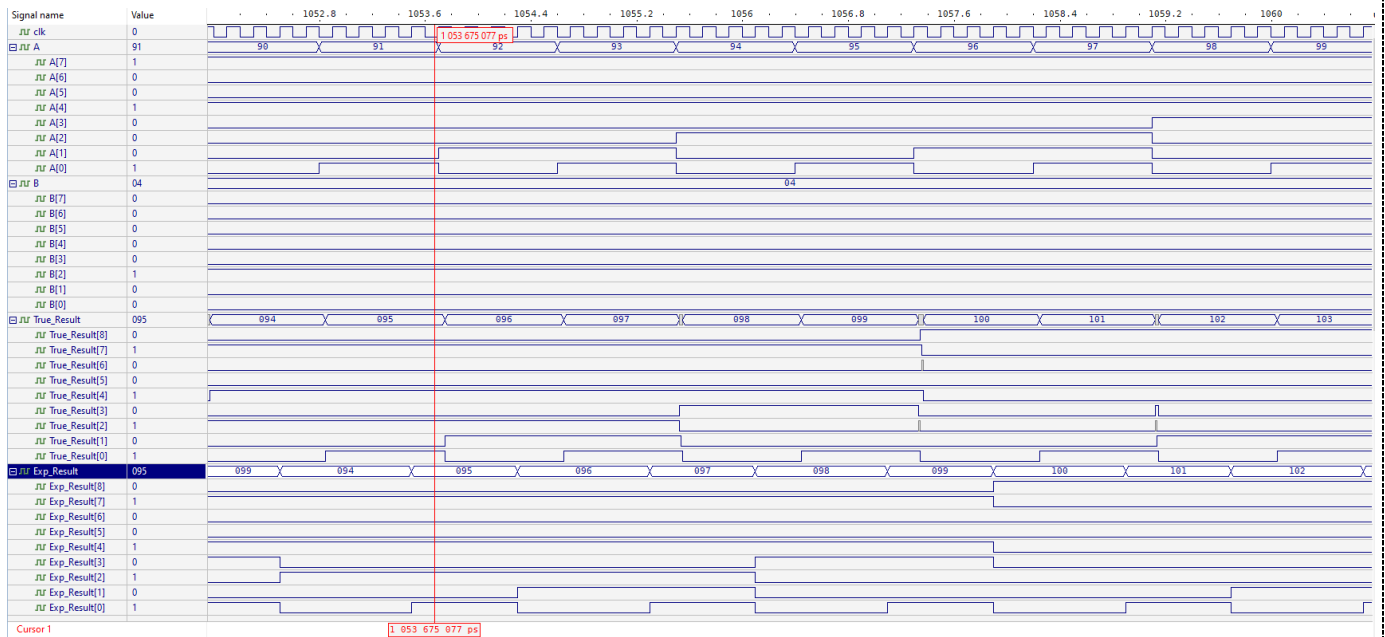

Conclusion

- We can construct any circuit, system, design we need in many ways.
- The small delays on and, or, xor....etc gates have a huge future effects on the results of the system design.
- Look ahead adders have more accurate, less delay results we get.

Appendix

```
module FA_1bit(A,B,Cin,Sum,Cout);

    input A,B,Cin;
    output Sum,Cout;
    wire w1,w2,w3;

    and #(8ns) (w1,A,B);
    xor  #(12ns) (w2,A,B);
    and #(8ns) (w3,w2,Cin);
    xor #(12ns) (Sum,w2,Cin);
    or  #(8ns) (Cout,w1,w3);

endmodule

////////////////////////////////////

module BinaryAdder_4bit(A,B,Cin,Sum,Cout);

    input [3:0] A,B;
    input Cin;
    output [3:0] Sum;
```

```
output Cout;  
wire C1,C2,C3;
```

```
FA_1bit F1(A[0],B[0],Cin,Sum[0],C1);  
FA_1bit F2(A[1],B[1],C1,Sum[1],C2);  
FA_1bit F3(A[2],B[2],C2,Sum[2],C3);  
FA_1bit F4(A[3],B[3],C3,Sum[3],Cout);
```

```
endmodule
```

```
////////////////////////////////////
```

```
module BCD_Adder1bit(A,B,Cin,F,OutputCarry);  
input [3:0] A,B;  
input Cin;  
output [3:0] F;  
output OutputCarry;  
wire [3:0] Z,S;  
wire k,w1,w2,w3;
```

```
BinaryAdder_4bit BA1(A,B,Cin,Z,k);
```

```
    and #(8ns) (w1,Z[2],Z[3]);
```

```
    and #(8ns) (w2,Z[1],Z[3]);
```

```
    or #(8ns) (OutputCarry,k,w1,w2);
```

```
    assign S = {1'b0,OutputCarry,OutputCarry,1'b0};
```

```
    BinaryAdder_4bit BA2(Z,S,0,F,w3);
```

```
endmodule
```

```
////////////////////////////////////
```

```
module dff(Q,D,clk);
```

```
    input D,clk;
```

```
    output reg Q;
```

```
    always @(posedge clk)
```

```
        begin
```

```
            Q <= D;
```

```
        end
```

```
endmodule
```


////////////////////////////////////

```
module Register_input(out,in,clk);
```

```
    output reg [7:0] out;
```

```
    input [7:0] in;
```

```
    input clk;
```

```
    wire [7:0] temp_out;
```

```
    dff d0(temp_out[0],in[0],clk);
```

```
    dff d1(temp_out[1],in[1],clk);
```

```
    dff d2(temp_out[2],in[2],clk);
```

```
    dff d3(temp_out[3],in[3],clk);
```

```
    dff d4(temp_out[4],in[4],clk);
```

```
    dff d5(temp_out[5],in[5],clk);
```

```
    dff d6(temp_out[6],in[6],clk);
```

```
    dff d7(temp_out[7],in[7],clk);
```

```
    always @ (posedge clk)
```

```
        begin
```

```
            out = temp_out;
```

```
        end
```

```
endmodule
```

////////////////////////////////////

```
module Register_output(out,in,clk);
```

```
    output reg [8:0] out;
```

```
    input [8:0] in;
```

```
    input clk;
```

```
    wire [8:0] temp_out;
```

```
    dff d0(temp_out[0],in[0],clk);
```

```
    dff d1(temp_out[1],in[1],clk);
```

```
    dff d2(temp_out[2],in[2],clk);
```

```
    dff d3(temp_out[3],in[3],clk);
```

```
    dff d4(temp_out[4],in[4],clk);
```

```
    dff d5(temp_out[5],in[5],clk);
```

```
    dff d6(temp_out[6],in[6],clk);
```

```
    dff d7(temp_out[7],in[7],clk);
```

```
    dff d8(temp_out[8],in[8],clk);
```

```
    always @ (posedge clk)
```

```
        begin
```

```
            out = temp_out;
```

```
        end
    endmodule

////////////////////////////////////
```

```
module System(A,B,clk,Result);
    input [7:0] A,B;
    reg Carryout;
    output reg [8:0] Result;
    reg [7:0] Aout,Bout;
    reg tempCout,tempCin;
    input clk;
    reg [3:0]SL,SM,AL,BL,AM,BM;
    reg [8:0] tempResult;

    Register_input IA(Aout,A,clk);
    Register_input IB(Bout,B,clk);

    assign AL = Aout[3:0];
    assign BL = Bout[3:0];
    assign AM = Aout[7:4];
```

```
assign BM = Bout[7:4];
```

```
BCD_Adder1bit D1(AL,BL,1'b0,SL,tempCout);
```

```
assign tempCin = tempCout;
```

```
BCD_Adder1bit D2(AM,BM,tempCin,SM,Carryout);
```

```
always @ (posedge clk)
```

```
begin
```

```
    assign tempResult = {Carryout,SM,SL};
```

```
end
```

```
Register_output O(Result,tempResult,clk);
```

```
endmodule
```

```
////////////////////////////////////
```

```
module BCD_Tester(A,B,Result);
```

```
input [7:0] A,B;  
output reg [8:0] Result;  
reg [7:0] Sum;  
reg Cout;
```

```
reg [3:0] AL,AM,BL,BM,SL,SM;  
reg temp_carry;  
reg [4:0] temp_SL,temp_SM;
```

```
assign AL = A[3:0];  
assign BL = B[3:0];  
assign AM = A[7:4];  
assign BM = B[7:4];
```

```
always @ (*)
```

```
begin  
    temp_SL = AL + BL + 0;
```

```
    if(temp_SL > 9)
```

```
        begin
```

```
temp_SL = temp_SL + 6;
```

```
temp_carry = 1;
```

```
SL = temp_SL[3:0];
```

```
end
```

```
else
```

```
begin
```

```
temp_carry = 0;
```

```
SL = temp_SL[3:0];
```

```
end
```

```
temp_SM = AM + BM + temp_carry;
```

```
if(temp_SM > 9)
```

```
begin
```

```
temp_SM = temp_SM + 6;
```

```
Cout = 1;
```

```
SM = temp_SM[3:0];
```

```
end
```

```
else
```

```
begin
```

```
Cout = 0;
```

```
SM = temp_SM[3:0];
```

```
end
```

```
Sum = {SM,SL};
```

```
#700ns    Result = {Cout,Sum};
```

```
end
```

```
endmodule
```

////////////////////////////////////

```
module Stage_1();
```

```
    reg [7:0] A,B;
```

```
    reg clk;
```

```
    wire [8:0] True_Result,Exp_Result;
```

```
    System S1(A,B,clk,Exp_Result); //Experimental Sum
```

```
    BCD_Tester T1(A,B,True_Result); //True Sum
```

```
    always #(100ns) clk = ~clk;
```

```
    initial
```

```
    begin
```

```
        clk = 0;
```

```
        {B,A} = 16'b0000000000000000;
```

```
        #700ns    {B,A} = 16'b0000000000000000;
```

```
        repeat(65535)
```



```
#(900ns) {B,A} = {B,A} + 16'b000000000000000001;
```

```
if(Exp_Result != True_Result)
```

```
begin
```

```
$display ("Error! at %b",True_Result);
```

```
end
```

```
end
```

```
endmodule
```

```
////////////////////////////////////
```

```
module carry_lookahead_adder_4_bit(i_add1, i_add2, o_result);
```

```
input [3:0] i_add1, i_add2;
```

```
output [4:0] o_result;
```

```
wire [4:0] w_C;
```

```
wire [3:0] w_G, w_P, w_SUM;
```

```
FA_1bit F1(.A(i_add1[0]), .B(i_add2[0]), .Cin(w_C[0]),  
.Sum(w_SUM[0]), .Cout());
```

```
FA_1bit F2(.A(i_add1[1]), .B(i_add2[1]), .Cin(w_C[1]),  
.Sum(w_SUM[1]), .Cout());
```

```
FA_1bit F3(.A(i_add1[2]), .B(i_add2[2]), .Cin(w_C[2]),  
.Sum(w_SUM[2]), .Cout());
```

```
FA_1bit F4(.A(i_add1[3]), .B(i_add2[3]), .Cin(w_C[3]),  
.Sum(w_SUM[3]), .Cout());
```

```
assign w_G[0] = i_add1[0] & i_add2[0];
```

```
assign w_G[1] = i_add1[1] & i_add2[1];
```

```
assign w_G[2] = i_add1[2] & i_add2[2];
```

```
assign w_G[3] = i_add1[3] & i_add2[3];
```

```
assign w_P[0] = i_add1[0] | i_add2[0];
```

```
assign w_P[1] = i_add1[1] | i_add2[1];
```

```
assign w_P[2] = i_add1[2] | i_add2[2];
```

```
assign w_P[3] = i_add1[3] | i_add2[3];
```

```
assign w_C[0] = 1'b0;
assign w_C[1] = w_G[0] | (w_P[0] & w_C[0]);
assign w_C[2] = w_G[1] | (w_P[1] & w_C[1]);
assign w_C[3] = w_G[2] | (w_P[2] & w_C[2]);
assign w_C[4] = w_G[3] | (w_P[3] & w_C[3]);
```

```
assign o_result = {w_C[4], w_SUM};
```

```
endmodule
```

```
////////////////////////////////////
```

```
module BCD_Adder_LA_1bit(A,B,F);
```

```
    input [3:0] A,B;
```

```
    output [4:0] F;
```

```
        reg [3:0] tempF;
```

```
        reg [3:0] Z,S;
```

```
        reg tempc;
```

```
    carry_lookahead_adder_4_bit BA1(A,B,S);
```

```
    always @(*)
```

```
if( S > 4'b1001)
    begin
        assign Z = 4'b0110;
        assign tempc = 1'b1;
    end
else
    begin
        assign Z = 4'b0000;
        assign tempc = 1'b0;
    end
end
```

```
carry_lookahead_adder_4_bit BA2(S,Z,tempF);
```

```
assign F={tempc,tempF};
```

```
endmodule
```

```
////////////////////////////////////
```

```
module BCD_Adder_LA_2bit(A,B,Result);
```

```
input [7:0] A,B;  
output [8:0] Result;  
reg [4:0] SL,SM;  
reg tens,hunds;
```

```
BCD_Adder_LA_1bit B1(A[3:0],B[3:0],SL);
```

```
assign tens = SL[4];
```

```
BCD_Adder_LA_1bit B2({A[7:4]+tens},B[7:4],SM);
```

```
assign hunds = SM[4];
```

```
assign Result = {hunds,SM[3:0],SL[3:0]};
```

```
endmodule
```

```
////////////////////////////////////
```

```
module Stage_2();
```

```
    reg [7:0] A,B;
```

```
reg clk;
wire [8:0] True_Result,Exp_Result;

System S1(A,B,clk,Exp_Result); //Experimental Sum
BCD_Adder_LA_2bit T1(A,B,True_Result);//True Sum

always #(100ns) clk = ~clk;

initial

begin

    clk = 0;
    {B,A} = 16'b0000000000000000;
    #700ns    {B,A} = 16'b0000000000000000;

    repeat(65535)

        #(900ns) {B,A} = {B,A} + 16'b0000000000000001;

        if(Exp_Result != True_Result)
```

begin

\$monitor ("Error! at %b",True_Result);

end

end

endmodule

////////////////////////////////////